
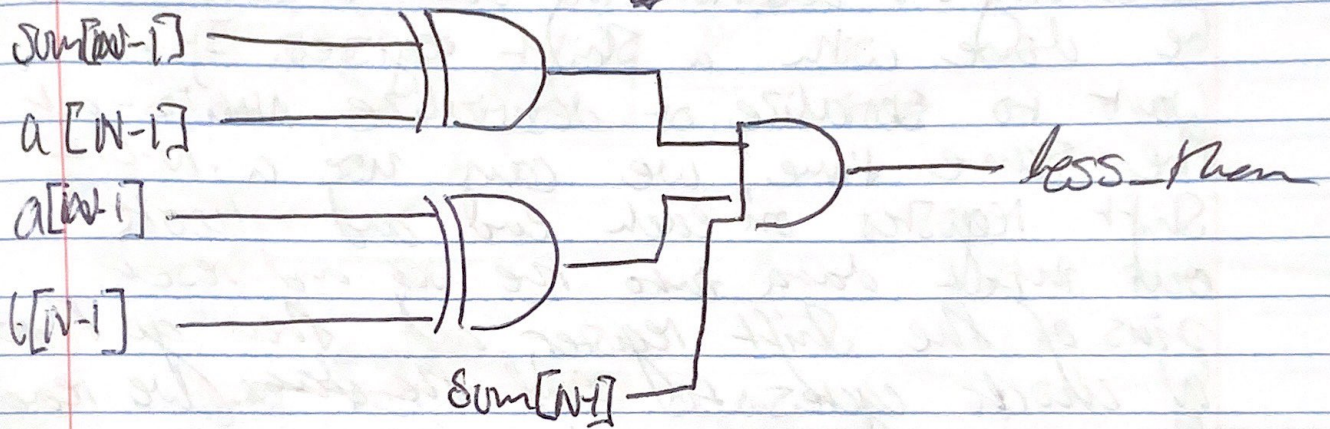


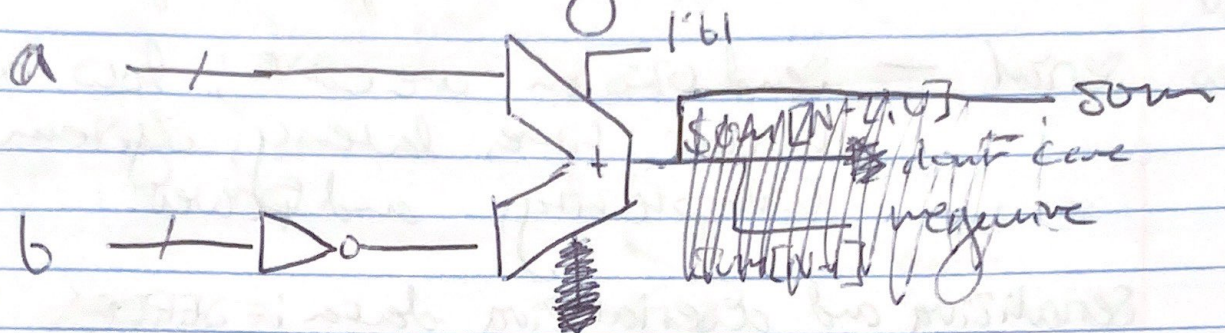2. We will implement  $a + \sim b + 1$  using an adder, NOT, and putting 1'b1 into the adder carry.






The second block checks if overflow is possible and if it may have happened!

- If  $a$  and  $b$  have the same sign,  
 $|a - b| \leq \max(a, b) < \text{maximum signed int magnitude}$ , so the difference cannot overflow. Thus, we need to look to the case where they can overflow! They have different signs!

- If since we're subtracting from  $a$ , and the difference should be within overflow, negative if  $a$  is negative since  $-b$  must be negative too, or positive if  $a$  is positive since  $-b$  must be positive. Thus, if the signs differ between  $a$  and the difference, we have overflowed. This gives the XOR.


If we've overflowed the sign will flip, so the sum must be positive to indicate a negative actual sum. If we haven't overflowed the sum must be negative. This gives the last XOR.

3. Pulse generator:

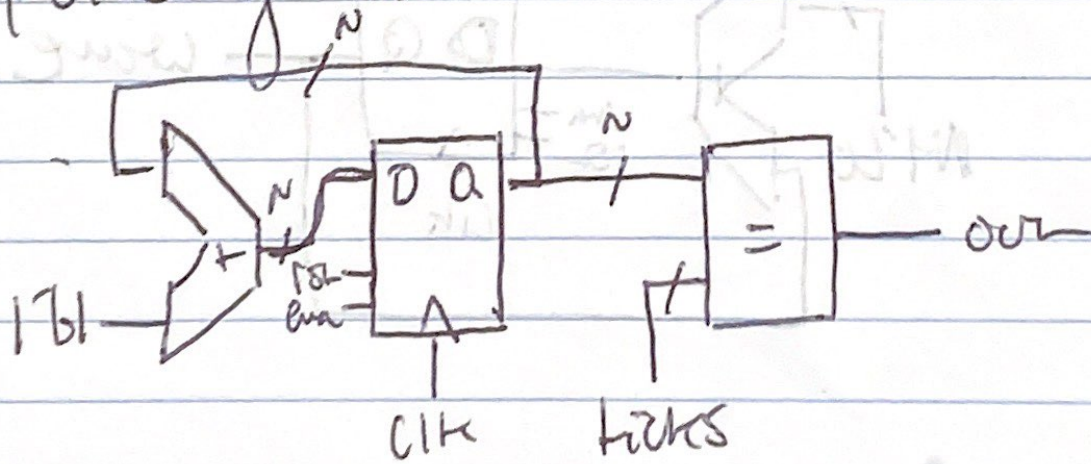



Triangle Wave!

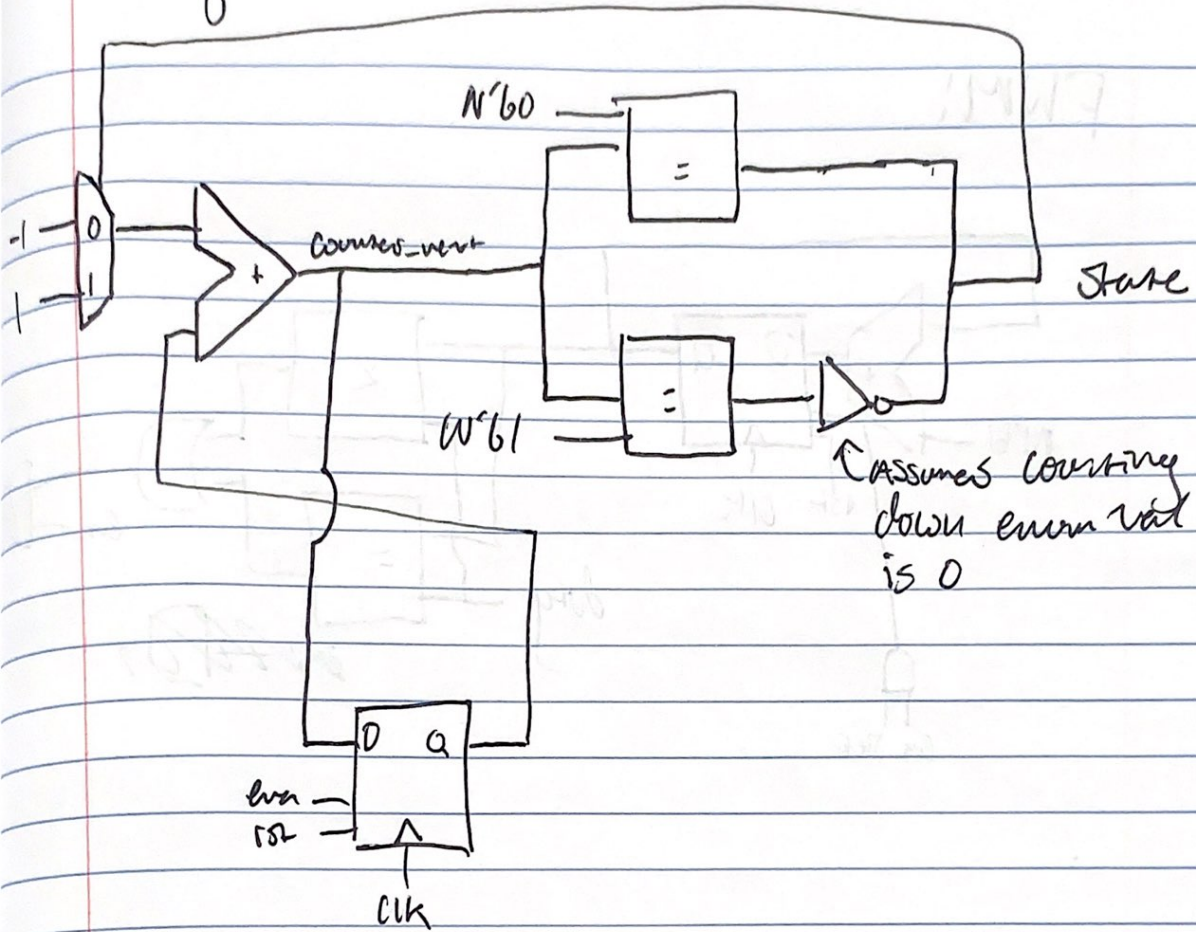

Triangle wave

PWM:

