

Collaborators:

## Homework 4


### 1. Reading and Review

- Continue referring back to Ch3, Ch4, and the Verilog Cheatsheet as needed
- Reread Ch1, 1.4.5, 1.4.6
- Chapter 5: 5.1 to 5.2.3
  - Section on Carry-Lookahead/Prefix Adders is optional

These questions are to make sure you get enough from the reading. Show your work!


 
#### a) Review: Flip Flops

Sketch the waveforms for the following circuit under different types of set/reset. Note that for this flip flop set and reset are active low (action occurs when the voltage is zero).





  iii) Assume reset is active high **and** synchronous. Sketch the waveforms for D and Q below.



## 2. Verilog Skillbuilding

### a) Verilog to Schematic

For each output, draw an equivalent gate level schematic (ands, ors, nots, xors, nands, nors, 2:1 muxes, flip flops) **\*and\*** write a phrase or sentence describing what that output does in terms of the inputs.

```
module mystery(a,b,c, out);
  input wire a, b, c;
  output logic out[3:0];
  always_comb begin
    out[0] = b ? a : c;
    out[1] = (~a & b) | (~b & a);
    out[2] = c | (b & c);
  end
  logic d;
  always_comb d = b ? a : 1'b0;
  always_ff @(posedge c) begin
    out[3] <= d;
  end
endmodule
```

